

# Digital Logic

# Logic

- **LOGIC DESIGN**
  - High level logical designs (programs) can be broken down into simple logical constructs
  - Boolean Algebra, Truth Tables and Electronic Logic Gates are all equivalent expressions
  - Expressions involve digital/binary/boolean logic
  - Gates are actual able to be implemented using high/low voltages (1/0)
- **Logic**
  - Combinational - no memory - output depends **ONLY** on current input
  - Sequential - includes state - memory

# Logic

- Truth Table
  - Lists all possible input combinations
  - n inputs
  - $2^n$  entries - lists all relevant outputs
  - 2 inputs - 4 entries
  - 3 inputs, 8 entries, etc...
  - Can completely describe ANY combinational logic function
  - Tables for AND ,OR, NOT, NAND, NOR,XOR

# Basic Components: Truth Tables

**AND**

| A | B | Out |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 1   |

**OR**

| A | B | Out |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 1   |

**NOT**

| A | Out |
|---|-----|
| 0 | 1   |
| 1 | 0   |

**NAND**

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

**NOR**


| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 0   |

**XOR**


| A | B | Out |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

# Basic Components: Logic Gates


## NAND Gate

 


## NOR Gate

 


## AND Gate

 

## OR Gate

 


# Basic Components: Gate

 

$C = A \vee B$  what kind of gate??

Note: can have multiple inputs ( $C = A + B + D$ )


# Basic Components: Gate

 

$C = A \cdot B$  what kind of gate??

Note: can have multiple inputs ( $C = A \cdot B \cdot D$ )

# Basic Components:NOT

 

| A | Out |
|---|-----|
| 0 | 1   |
| 1 | 0   |

**NOT Gate**

# Logic

- Boolean Algebra
- Logic equations
- All variables = either 0 or 1
- 3 basic operators
- **AND,  $\bullet$**
- **OR,  $+$**
- **NOT,  $\neg$**
- Can derive
- XOR, NAND, NOR

# Logic

- COMBINATIONAL LOGIC
- Simple logical expressions
- Can Create an exclusive or from the 3 basic gates
  - (and, or, not)
  - Do it!
    - draw gates

XOR truth table

| A | B | Out |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

# Logic

- COMBINATIONAL LOGIC
- Simple logical expressions
- Can Create an exclusive or from the 3 basic gates
- Using only the rows where result is 1
  - $(\text{not } A) \text{ and } B) \text{ or } (A \text{ and } (\text{not } B) )$

# Logic

- How did we get an XOR as
  - $((\text{not } A) \text{ and } B) \text{ or } (A \text{ and } (\text{not } B))$  ???

| A | B | Out |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 1   |
| 1 | 0 | 1   |
| 1 | 1 | 0   |

XOR

Look at the two rows where Out = 1...  
When is Out == 1??

1. When A is 0 (not A) and B is 1  
[we can write as:  $((\text{not } A) \text{ and } B)$ ]  
OR

2. When A is 1 and B is 0 (not B)  
[we can write as:  $(A \text{ and } (\text{not } B))$ ]

so.....

$((\text{not } A) \text{ and } B) \text{ or } (A \text{ and } (\text{not } B))$

# Logic

- Can find any equation for any truth table

ABC D

000 1 = ( $\neg A \cdot \neg B \cdot \neg C$ )

001 0

010 1 = ( $\neg A \cdot B \cdot \neg C$ )

011 0

100 0

101 0

110 1 = ( $A \cdot B \cdot \neg C$ )

111 0

# Logic: Sum of Products

$$(\neg A \cdot \neg B \cdot \neg C) + (\neg A \cdot B \cdot \neg C) + (A \cdot B \cdot \neg C)$$

ABC D

000 1 = ( $\neg A \cdot \neg B \cdot \neg C$ )

001 0

010 1 = ( $\neg A \cdot B \cdot \neg C$ )

011 0

100 0

101 0

110 1 = ( $A \cdot B \cdot \neg C$ )

111 0

# Logic: Sum of Products

| <u>ABC</u> | <u>D</u> |
|------------|----------|
|------------|----------|

|     |   |
|-----|---|
| 000 | 1 |
|-----|---|

|     |   |
|-----|---|
| 001 | 0 |
|-----|---|

|     |   |
|-----|---|
| 010 | 0 |
|-----|---|

|     |   |
|-----|---|
| 011 | 0 |
|-----|---|

|     |   |
|-----|---|
| 100 | 0 |
|-----|---|

|     |   |
|-----|---|
| 101 | 1 |
|-----|---|

|     |   |
|-----|---|
| 110 | 0 |
|-----|---|

|     |   |
|-----|---|
| 111 | 0 |
|-----|---|

Create boolean expression for this truth table.

Create a logic diagram using gates.

# Logic: Sum of Products

| <u>ABC</u> | <u>D</u> |
|------------|----------|
|------------|----------|

|     |   |
|-----|---|
| 000 | 1 |
|-----|---|

|     |   |
|-----|---|
| 001 | 0 |
|-----|---|

|     |   |
|-----|---|
| 010 | 0 |
|-----|---|

|     |   |
|-----|---|
| 011 | 0 |
|-----|---|

|     |   |
|-----|---|
| 100 | 0 |
|-----|---|

|     |   |
|-----|---|
| 101 | 1 |
|-----|---|

|     |   |
|-----|---|
| 110 | 0 |
|-----|---|

|     |   |
|-----|---|
| 111 | 0 |
|-----|---|

Create boolean expression for this truth table.

$$(\neg A \bullet \neg B \bullet \neg C) + (A \bullet \neg B \bullet C)$$

Create a logic diagram using gates.

# Logic: XOR

- BreadBoard Software


- Create an XOR  $((\text{not } A) \text{ and } B) \text{ or } (A \text{ and } (\text{not } B))$
- Need two and gates and an or gate

$$((\neg A) \cdot B) + (A \cdot (\neg B))$$


Due \_\_\_\_\_ by midnight

# Logic: NAND


- NAND gates can implement ANY logic

 

NOT

 

AND

 

OR

- Cheap and fast

# Logic: Half adder

- Binary addition
- A simple half adder
- truth table

| <u>A</u> | <u>B</u> | <u>C<sup>o</sup></u> | <u>S</u> |
|----------|----------|----------------------|----------|
| • 0      | 0        | 0                    | 0        |
| • 0      | 1        | 0                    | 1        |
| • 1      | 0        | 0                    | 1        |
| • 1      | 1        | 1                    | 0        |

Create a boolean expression for a half adder using sum of products.

Carry

Sum

# Logic: Half adder

- Binary addition
- A simple half adder
- truth table

| <u>A</u> | <u>B</u> | <u>C<sup>o</sup></u> | <u>S</u> |
|----------|----------|----------------------|----------|
| 0        | 0        | 0                    | 0        |
| 0        | 1        | 0                    | 1        |
| 1        | 0        | 0                    | 1        |
| 1        | 1        | 1                    | 0        |

Create a boolean expression for a half adder using sum of products.

**Carry**

(A and B)

**Sum**

(A and (not B)) or ((not A) and B)

# Logic: Half Adder

- Binary addition
- A simple half adder
- truth table

| <u>A</u> | <u>B</u> | <u>C<sup>o</sup></u> | <u>S</u> |
|----------|----------|----------------------|----------|
| 0        | 0        | 0                    | 0        |
| 0        | 1        | 0                    | 1        |
| 1        | 0        | 0                    | 1        |
| 1        | 1        | 1                    | 0        |

Create a boolean expression for a half adder using sum of products.

**Carry**

(A and B)

**Sum**

(A and (not B)) or ((not A) and B)

**Using gates, create a half adder!**

**If each gate is 20ns, what's the fastest clock?**

# Logic: Half Adder

- BreadBoard Software
- Create a Half Adder
  - **Carry**
  - (A and B)
  - **Sum** Half.wbd
  - (A and (not B)) or ((not A) and B)
  - May use XOR gates for this
  - Due \_\_\_\_\_ @ 11

# Logic: Full Adder

- Truth Table for a full adder (w/carry in)

| <u>ABCi</u> | <u>Co</u> | <u>Sum</u> |
|-------------|-----------|------------|
| 000         | 0         | 0          |
| 001         | 0         | 1          |
| 010         | 0         | 1          |
| 011         | 1         | 0          |
| 100         | 0         | 1          |
| 101         | 1         | 0          |
| 110         | 1         | 0          |
| 111         | 1         | 1          |

# Logic: Full Adder

- Truth Table for a full adder (w/carry in)

| <u>ABCi</u> | <u>Co</u> | <u>Sum</u> |
|-------------|-----------|------------|
| 000         | 0         | 0          |
| 001         | 0         | 1          |
| 010         | 0         | 1          |
| 011         | 1         | 0          |
| 100         | 0         | 1          |
| 101         | 1         | 0          |
| 110         | 1         | 0          |
| 111         | 1         | 1          |

Create a boolean expression for Co and Sum

# Logic: Full Adder

- Truth Table for a full adder (w/carry in)

| <u>ABCi</u> | <u>Co</u> | <u>Sum</u> |
|-------------|-----------|------------|
| 000         | 0         | 0          |
| 001         | 0         | 1          |
| 010         | 0         | 1          |
| 011         | 1         | 0          |
| 100         | 0         | 1          |
| 101         | 1         | 0          |
| 110         | 1         | 0          |
| 111         | 1         | 1          |


Create a boolean expression for Co and Sum

Now create a digital circuit that will implement that expression...

Is there a problem??
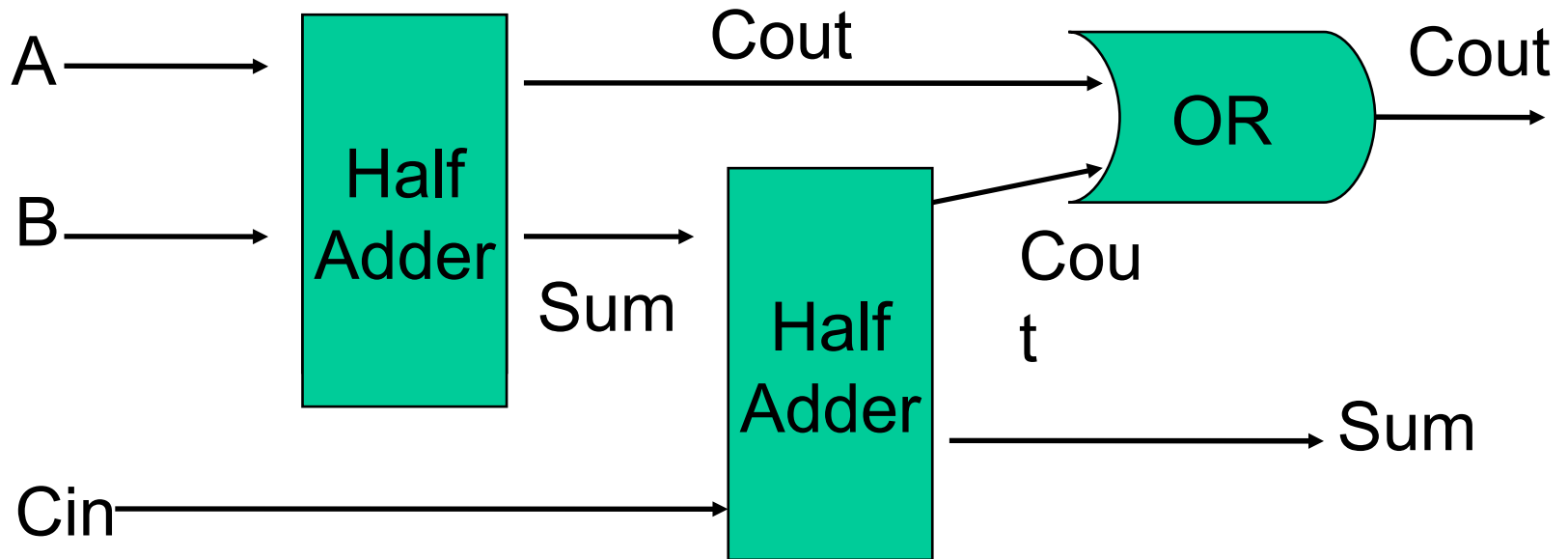
# Logic

- Combining half adders to make a full adder



# Logic: Full Adder

- BreadBoard Software
- Implement the 4 bit full Adder
  - C0 is the Carry IN
  - C4 is the Carry OUT
  - 16 pins : pin 16 is Vcc, pin 8 is GRND
  - output to 7 segment display
  - detect unsigned overflow
- Due \_\_\_\_\_ @ 10

Full.wbd

# Logic: Worksheet


- Problem: Consider a logic function with three inputs: A, B, and C.
  - Output D is true if at least one input is true
  - Output E is true if exactly two inputs are true
  - Output F is true only if all three inputs are true
- Show the truth table for these three functions.
- Show the Boolean equations for these three functions.  
Show an implementation consisting of inverters, AND, and OR gates.

# Logic: Worksheet

- Worksheet
- DeMorgan's Law states that
  - $\text{NOT } (a \text{ OR } b) = (\text{NOT } a) \text{ AND } (\text{NOT } b)$
  - Prove it with a truth table
  - Show equivalent digital logic using gates
- DeMorgan's Law states that
  - $a \text{ AND } (b \text{ OR } c) = (a \text{ AND } b) \text{ OR } (a \text{ AND } c)$
  - Prove it with a truth table
  - Show equivalent digital logic using gates

 
# Logic: Worksheet

- Worksheet
  - create truth table and boolean expression


 
# The Multiplexor

- Selects one of the inputs (A or B) to be the output, based on a control input




***note: we call this a 2-input mux  
even though it has 3 inputs!***



How many bits does S have to be to select  
1 of 2 things? 3 things? 4? 5? 6? 8? 10?
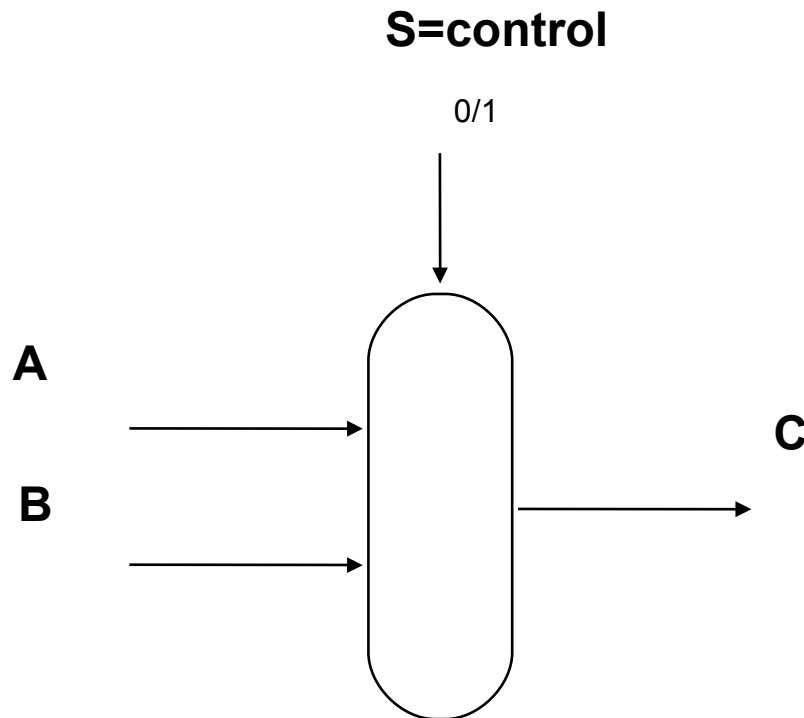
# The Multiplexor

- If  $A = 01101111$  and  $B = 00000001$  and  $S = 1$   
what will  $C$  be??




# Tricks to Reduce Cycle Time

  

- Reduce the number of gate levels
- Faster Gates

# S-R Latch: Memory

 

NOR

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 0   |

- Sequential Logic
- When neither R or S are asserted then the previous value is stored
- R=1 (clear), then Q=0 / S=1(set), then Q=1

**Time**

# Execution Time

- Elapsed Time
  - counts everything (*disk and memory accesses, I/O , other programs executing, etc.*)
  - a useful number, but often not good for comparison purposes
- CPU time
  - doesn't count I/O or time spent running other programs
  - can be broken up into *system CPU time*, and *user CPU time*
- Our focus: *user CPU time*
  - time spent executing the lines of code that are "in" our program
  - not OS overhead - not other jobs while we wait
  - how do we measure??

# Clock Cycles

- How do we measure time?
  - Clock cycle
    - time can be expressed as a series of clock ticks
    - a clock is the sequencing, stepping mechanism which is the smallest unit in which a hardware event can take place
    - each tick of the clock is called a CLOCK CYCLE or period
    - a cycle is measured as some fraction of a second (1  $\mu$ s or 100 ns)

# Clock Cycles


- **CLOCK RATE** measures how many times a clock ticks *per second*
  - a clock cycle is measured as the inverse of the clock rate
  - 1 hz is a single sine wave taking 1 second
  - if cycle = 1 second, rate = 1 hz
- A 100 hz clock is 100 waves in a single second with each cycle taking .01 sec .
  - So, cycle=.01, rate = 100 hz
- A 1 megahertz (1 mhz) clock ticks a million times per second
  - 1 million hz is a million waves in a sec each taking .000001 or 1 microsecond

# Clock Cycles

- .000 000 000 000
- milli micro nano pico
- A 1 mhz clock has a 1/1million cycle = .000 001
- A 10 mhz clock has a 1/10million cycle = .000 000 100
- A 100 mhz clock has a 1/100million cycle = .000 000 010
- Why slow clocks?
  - electricity takes real time to travel
  - gates take real time to traverse
  - must allow signals to be stable in the slowest circuit
  - can't tick until outputs of one circuit are stable and can act as the inputs to the next
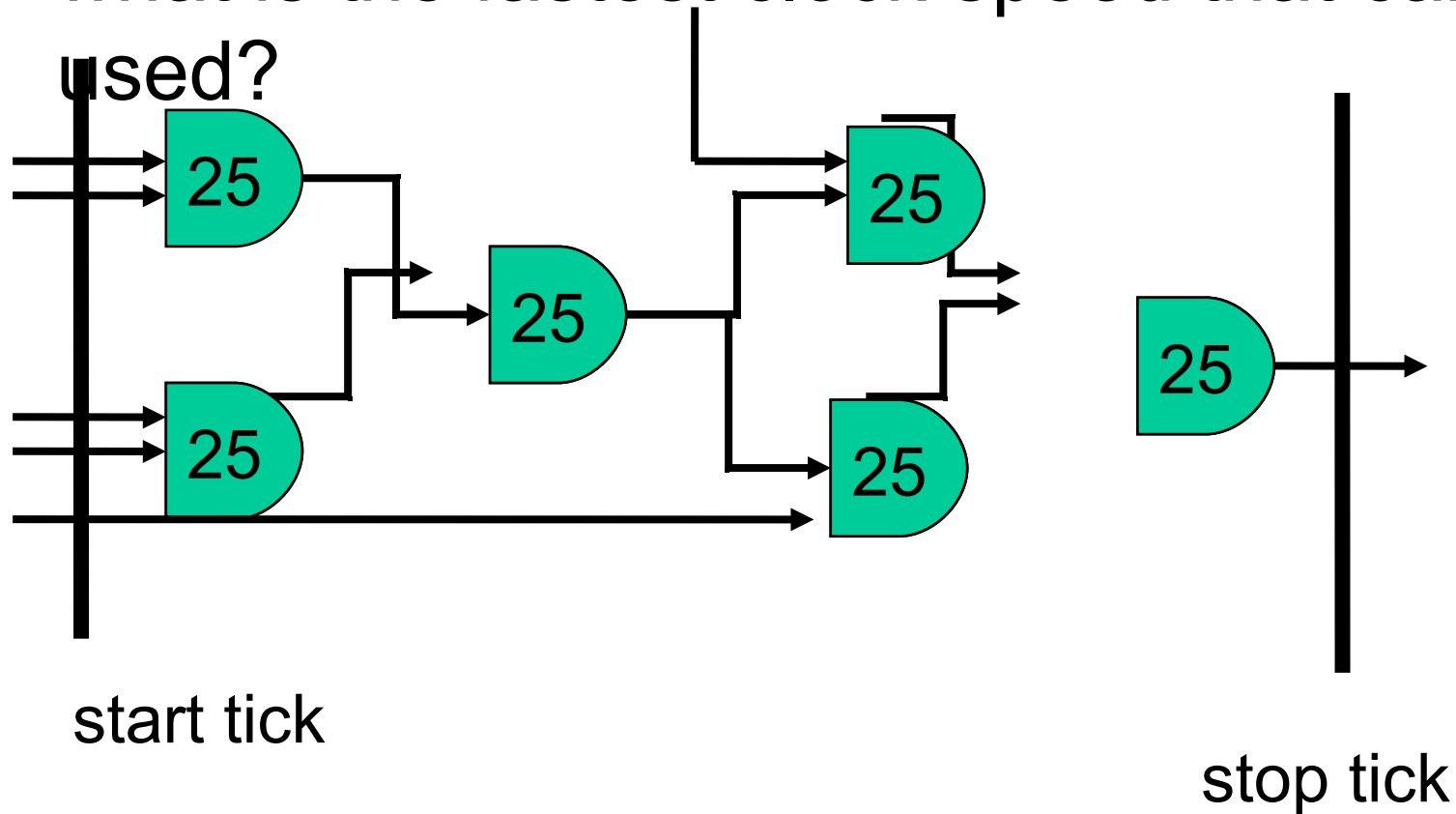
# Clock Cycles

- If each AND gate takes 25ns to traverse, what is the fastest clock speed that can be used?



# Clock Cycles

- Summary:
- Cycle time = length of a single clock tick = seconds per cycle (100 Hz = .001 cycle)
- Clock rate (frequency) = cycles per second (100 Hz. = 100 cycle/sec)
- **Clock rate is INVERSE of Clock cycle**
- A 200 Mhz. clock has a cycle time of:
  - ?
- A machine with a cycle time of 100 ns
  - ?

# How to Improve Performance

- Instead of reporting execution time in seconds, we often use cycles
- Clock “ticks” indicate when to start activities (one abstraction):
- So, to improve performance (everything else being equal) you can either:
  - \_\_\_\_\_ the # of required cycles for a program,
  - or
  - \_\_\_\_\_ the clock cycle time or, said another way,
  - \_\_\_\_\_ the clock rate.

# Example

- Execution time of the application program ultimately it is simply the number of clock cycles for a program x cycle time

example:

1. a program takes 300 clock cycles to execute
2. each cycle is 10 ns
3.  $300 \times 10 \text{ ns} = 3000 \text{ ns} = 3 \text{ microseconds}$

example:

cycle time is a given for a system (486/33mhz)

how do you find number of clock cycles??

1. find the number of instructions executed
2. find the average clock cycles per instruction (**CPI**)
3.  $\text{time} = \text{CPI} \times (\text{cycle time}) \times (\# \text{ of instructions})$

# Example

## Now that we understand cycles

- A given program will require
  - some number of instructions (machine instructions)
  - some number of cycles
  - some number of seconds

# Example

## Now that we understand cycles

- We have a vocabulary that relates these quantities:
  - cycle time (seconds per cycle)
  - clock rate (cycles per second)
  - CPI (cycles per instruction)  
*a floating point intensive application might have a higher CPI*
  - MIPS (millions of instructions per second)  
*this would be higher for a program using simple instructions*

# QUIZ

- 3 inputs: A, B, C
- There are 2 outputs: D, E
- D is True whenever only A & B are True
- E is True whenever C is False
- Create a truth table
- Create a boolean expression using "sum of products"
- Create a logic gate diagram directly from the boolean expression (And, Or, Not)

Don't Simplify Anything  
but MAY use 3 input gates

# CPI Example

- Suppose we have two implementations of the same instruction set architecture (ISA).
- For some program with 100 instructions:
  - Machine A has a clock cycle time of 10 ns. and a CPI of 2.0
  - Machine B has a clock cycle time of 20 ns. and a CPI of 1.2
  - What machine is faster for this program, and by how much?
  - *If two machines have the same ISA which of our quantities (e.g., clock rate, CPI, execution time, # of instructions, MIPS) will always be identical?*

# Worksheet

## **CIS 350 Architecture Worksheet #1      Performance**

1. What is the clock speed of a clock with a period of 10 ns? 20 ns? 100 ns?
2. A clock running at the speed of 25 Mhz has a cycle of? 33 Mhz? 66 Mhz?
3. The execution time of a program depends on three things: what are those three things?

# Worksheet

## CIS 350 Architecture Worksheet #1 Performance

1. What is the clock speed of a clock with a period of 10 ns? 20 ns? 100 ns?

100MHz, 50 MHz, 10 MHz

2. A clock running at the speed of 25 Mhz has a cycle of? 33 Mhz? 66 Mhz?

40 ns, 30.30ns, 15.15 ns

3. The execution time of a program depends on three things: what are those three things?

# instructions, cycles per instruction, cycle time

# Worksheet

## **CIS 350 Architecture Worksheet #1      Performance**

4. A benchmark with 100,000 instructions is being run on your new CPU. To have the fastest performance on this benchmark do you choose:

- a. a CPI of 1.7 and a clock cycle of 19 ns
- b. a CPI of 2.4 and a clock speed of 75 Mhz

5. Draw a diagram of a length of one second showing a clock speed of 5 hz. Label the length of each cycle. Calculate the length of a program with 100 instructions and a CPI of 1.

# Worksheet

## CIS 350 Architecture Worksheet #1 Performance

4. A benchmark with 100,000 instructions is being run on your new CPU. To have the fastest performance on this benchmark do you choose:

a. a CPI of 1.7 and a clock cycle of 19 ns

$$1.7 \times 19\text{ns} \times 100,000 = 3,230,000\text{ns} = 3,230\text{us} = 3.23\text{ms}$$

b. a CPI of 2.4 and a clock speed of 75 Mhz

$$2.4 \times 13\text{ns} \times 100,000 = 3,120,000\text{ns} = 3,120\text{us} = 3.12\text{ms}$$

5. Draw a diagram of a length of one second showing a clock speed of 5 hz. Label the length of each cycle.

Calculate the length of a program with 100 instructions and a CPI of 1.  $\text{cycle} = .2 \times 100 \times 1 = 20\text{sec}$

# # of Instructions Example

- A compiler designer is trying to decide between two code sequences for a particular machine. Based on the hardware implementation, there are three different classes of instructions: *Class A*, *Class B*, and *Class C* that require one, two, and three cycles respectively.
- The first code sequence has **5 instructions**: 2 of A, 1 of B, and 2 of C
- The second sequence has **6 instructions**: 4 of A, 1 of B, and 1 of C.
- Which sequence will be faster? How much? What is the CPI for each sequence?

# # of Instructions Example

- A compiler designer is trying to decide between two code sequences for a particular machine. Based on the hardware implementation, there are three different classes of instructions: *Class A*, *Class B*, and *Class C* that require one, two, and three cycles respectively.
- The first code sequence has **5 instructions**: 2 of A, 1 of B, and 2 of C ( $2+2+6 = 10$  cycles / 5 inst = 2.0 cpi)
- The second sequence has **6 instructions**: 4 of A, 1 of B, and 1 of C. ( $4+2+3 = 9$  cycles / 6inst = 1.5 cpi)
- Which sequence will be faster? How much?  
What is the CPI for each sequence?

# MIPS example

- Two different compilers are being tested for a 100 MHz. machine with three different classes of instructions: Class A, Class B, and Class C, which require one, two, and three cycles (respectively). Both compilers are used to produce code for a large piece of software.

The first compiler's code uses 5 million Class A instructions, 1 million Class B instructions, and 1 million Class C instructions.

The second compiler's code uses 10 million Class A instructions, 1 million Class B instructions, and 1 million Class C instructions.

- Which sequence will be faster according to MIPS?
- Which sequence will be faster according to execution time?

# MIPS example

- Two different compilers are being tested for a 100 MHz. machine with three different classes of instructions: Class A, Class B, and Class C, which require one, two, and three cycles (respectively). Both compilers are used to produce code for a large piece of software.
- The first compiler's code uses 5 million Class A instructions, 1 million Class B instructions, and 1 million Class C instructions.  
[10m cycles (faster) 7m inst
- The second compiler's code uses 10 million Class A instructions, 1 million Class B instructions, and 1 million Class C instructions.  
[15m cycles (slower) 12m inst (but more inst. over given time)
- Which sequence will be faster according to MIPS?
- Which sequence will be faster according to execution time?

# Amdahl's Law

Execution Time After Improvement =  
Execution Time Unaffected + ( Execution Time  
Affected / Amount of Improvement )

- Example: "Suppose a program runs in 100 seconds on a machine, with multiply responsible for 80 seconds of this time. How much do we have to improve the speed of multiplication if we want the program to run 4 times faster?"
- How about 5 times faster?
- *Principle: Make the common case fast*